

1) A)

A	B	C	S1(Tranca)	S2(Bomba)	S3(Válvula)
0	0	0	0	0	1
0	0	1	0	0	0
0	1	0	0	1	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	0	0
1	1	0	0	1	0
1	1	1	0	0	0

Variáveis de entrada: A, B, C. Variáveis de saída: S1, S2, S3.

B)

	B'C'	B'C	BC	BC'
A'	0	0	0	0
A	1	1	0	0

$S1 = A \cdot B'$


	B'C'	B'C	BC	BC'
A'	0	0	0	1
A	0	0	0	1

$S2 = BC'$

	B'C'	B'C	BC	BC'
A'	1	0	0	0
A	1	0	0	0

$S3 = B'C'$

C)

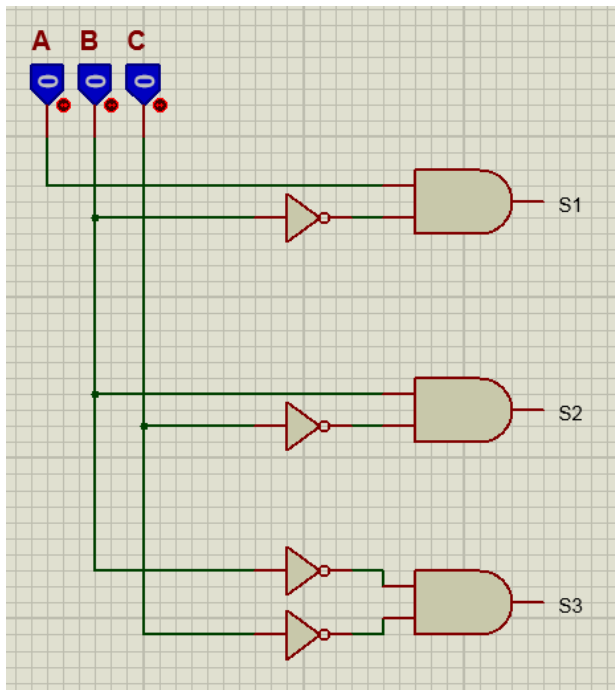

D) Modulo:


```
24  -- arithmetic functions with Signed or Unsigned values
25  --use IEEE.NUMERIC_STD.ALL;
26
27  -- Uncomment the following library declaration if instantiating
28  -- any Xilinx primitives in this code.
29  --library UNISIM;
30  --use UNISIM.VComponents.all;
31
32  entity modulo is
33      Port ( A : in  STD_LOGIC;
34            B : in  STD_LOGIC;
35            C : in  STD_LOGIC;
36            S1 : out STD_LOGIC;
37            S2 : out STD_LOGIC;
38            S3 : out STD_LOGIC);
39  end modulo;
40
41  architecture Behavioral of modulo is
42
43  begin
44
45      S1<= (A AND (NOT B));
46      S2<= (B AND (NOT C));
47      S3<= ((NOT B) AND (NOT C));
48
49  end Behavioral;
50
51
```

Teste:

```

81  -- Stimulus process
82  stim_proc: process
83  begin
84
85      wait for 100 ns;
86      A<= '0';
87      B<= '0';
88      C<= '0';
89      -- 001
90      wait for 100 ns;
91      A<= '0';
92      B<= '0';
93      C<= '1';
94      -- 010
95      wait for 100 ns;
96      A<= '0';
97      B<= '1';
98      C<= '0';
99      -- 011
100     wait for 100 ns;
101     A<= '0';
102     B<= '1';
103     C<= '1';
104     -- 100
105     wait for 100 ns;
106     A<= '1';
107     B<= '0';
108     C<= '0';
109
110     -- 101
111     wait for 100 ns;
112     A<= '1';
113     B<= '0';
114     C<= '1';
115     -- 110
116     wait for 100 ns;
117     A<= '1';
118     B<= '1';
119     C<= '0';
120     -- 111
121     wait for 100 ns;
122     A<= '1';
123     B<= '1';
124     C<= '1';
125     -- 000
126     wait for 100 ns;
127     A<= '0';
128     B<= '0';
129     C<= '0';
130
131     wait;
132     end process;
133 END;
```

Gráfico:

 

2)A) Variáveis de entrada: A, B, C. Variáveis de saída: S

B)


A	B	C	S
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

C)

	B'C'	B'C	BC	BC'
A'	0	0	1	0
A	0	1	1	1

$S = AC + AB + BC$

D)

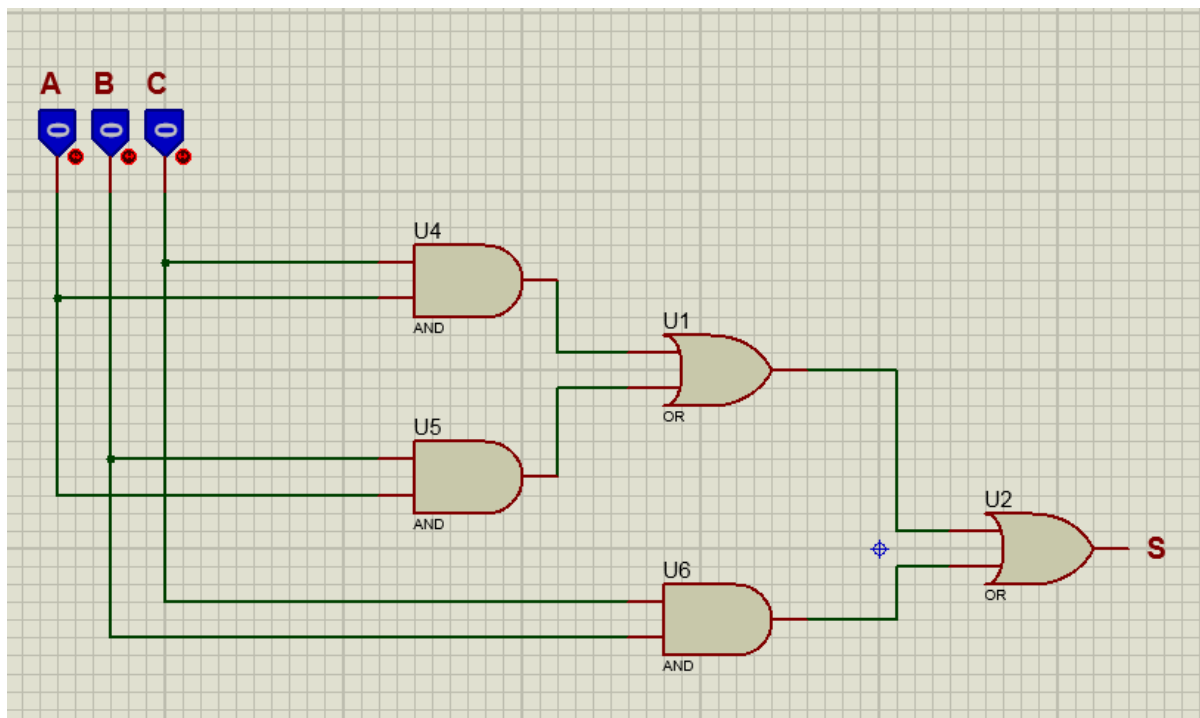

# E)Modulo:

```


21 use IEEE.STD_LOGIC_1164.ALL;
22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity modulo is
33     Port ( A : in  STD_LOGIC;
34           B : in  STD_LOGIC;
35           C : in  STD_LOGIC;
36           S : out STD_LOGIC);
37
38 end modulo;
39
40 architecture Behavioral of modulo is
41
42 begin
43
44     S<= (A AND C) OR (A AND B) OR (B AND C);
45
46 end Behavioral;
47
48

```

# Teste:

77	stim_proc: process	101	A<= '1';
78	begin	102	B<= '0';
79		103	C<= '0';
80	wait for 100 ns;	104	-- 101
81	A<= '0';	105	wait for 100 ns;
82	B<= '0';	106	A<= '1';
83	C<= '0';	107	B<= '0';
84	-- 001	108	C<= '1';
85	wait for 100 ns;	109	-- 110
86	A<= '0';	110	wait for 100 ns;
87	B<= '0';	111	A<= '1';
88	C<= '1';	112	B<= '1';
89	-- 010	113	C<= '0';
90	wait for 100 ns;	114	-- 111
91	A<= '0';	115	wait for 100 ns;
92	B<= '1';	116	A<= '1';
93	C<= '0';	117	B<= '1';
94	-- 011	118	C<= '1';
95	wait for 100 ns;	119	-- 000
96	A<= '0';	120	wait for 100 ns;
97	B<= '1';	121	A<= '0';
98	C<= '1';	122	B<= '0';
99	-- 100	123	C<= '0';
100	wait for 100 ns;	124	
101	A<= '1';	125	wait;
102	B<= '0';	126	end process;
103	C<= '0';	127	
104	-- 101	128	END;

Gráfico:

 

$$3) S = [(AB+D)' + (CD)'] + [(B' + (ADBC)' + DD)']$$

Modulo:

```

22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity modulo is
33     Port ( A : in  STD_LOGIC;
34           B : in  STD_LOGIC;
35           C : in  STD_LOGIC;
36           D : in  STD_LOGIC;
37           S : out STD_LOGIC);
38
39 end modulo;
40
41 architecture Behavioral of modulo is
42
43 begin
44
45     S<= (((NOT((A AND B)OR D)) OR (NOT(C AND D))) OR (((NOT B) OR (NOT(A AND D AND B AND C))) OR (NOT(D AND D))));
46
47 end Behavioral;
48
49

```

Teste:

```

79  stim_proc: process
80  begin
81
82      wait for 100 ns;
83      A<= '0';
84      B<= '0';
85      C<= '0';
86      D<= '0';
87      -- 0001
88      wait for 100 ns;
89      A<= '0';
90      B<= '0';
91      C<= '0';
92      D<= '1';
93      -- 0010
94      wait for 100 ns;
95      A<= '0';
96      B<= '0';
97      C<= '1';
98      D<= '0';
99      -- 0011
100     wait for 100 ns;
101     A<= '0';
102     B<= '0';
103     C<= '1';
104     D<= '1';
105     -- 0100
106     wait for 100 ns;
160     -- 1101
161     wait for 100 ns;
162     A<= '1';
163     B<= '1';
164     C<= '0';
165     D<= '1';
166     -- 1110
167     wait for 100 ns;
168     A<= '1';
169     B<= '1';
170     C<= '1';
171     D<= '0';
172     -- 1111
173     wait for 100 ns;
174     A<= '1';
175     B<= '1';
176     C<= '1';
177     D<= '1';
178     -- 0000
179     wait for 100 ns;
180     A<= '0';
181     B<= '0';
182     C<= '0';
183     D<= '0';
184     wait;
185 end process;
186
187 END;

```

Gráfico:

