

## INATEL - Instituto Nacional de Telecomunicações

E207 – Eletrônica Digital I

3º Período / 1º Semestre de 2021

**Professores:** Bruno de Oliveira Monteiro

[bruno@inatel.br](mailto:bruno@inatel.br)

**Monitores:**

Felipe Pereira Silveira

[felipepereira@gea.inatel.br](mailto:felipepereira@gea.inatel.br)

Carlos Daniel Borges Vilela Marques  
Gualter Machado Mesquita

[carlos.marques@gea.inatel.br](mailto:carlos.marques@gea.inatel.br)

[machadomgualter@gmail.com](mailto:machadomgualter@gmail.com)

Isabela Rezende Barbosa da Silva  
Maíra Alves Chagas  
Pedro Henrique Praxedes dos Reis  
Thalita Fortes Domingos

[isabela.r@gec.inatel.br](mailto:isabela.r@gec.inatel.br)

[mairaalves@gec.inatel.br](mailto:mairaalves@gec.inatel.br)

[pedro.reis@gea.inatel.br](mailto:pedro.reis@gea.inatel.br)

[thalita.fortes@gec.inatel.br](mailto:thalita.fortes@gec.inatel.br)

**Aluno:** \_

**Matrícula:** \_

**Período:** \_

**Data:** \_

\_ / \_ / \_

### RELATÓRIO 5 RESOLUÇÃO

**EXERCÍCIO**

**Questão 1.**

**Módulo**

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Questaol is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          Sand : out  STD_LOGIC;
          Sor : out  STD_LOGIC;
          Sxor : out  STD_LOGIC;
          Sxnor : out  STD_LOGIC;
          SnotA : out  STD_LOGIC;
          SnotB : out  STD_LOGIC);
end Questaol;

architecture Behavioral of Questaol is

begin

Sand <= A and B;
Sor <= A or B;
Sxor <= A xor B;
Sxnor <= A xnor B;
SnotA <= not (A);
SnotB <= not (B);

end Behavioral;

```

Teste

```

41
42 COMPONENT Questao1
43 PORT(
44     A : IN  std_logic;
45     B : IN  std_logic;
46     Sand : OUT std_logic;
47     Sor : OUT std_logic;
48     Sxor : OUT std_logic;
49     Sxnor : OUT std_logic;
50     SnotA : OUT std_logic;
51     SnotB : OUT std_logic
52 );
53 END COMPONENT;
54
55
56 --Inputs
57 signal A : std_logic := '0';
58 signal B : std_logic := '0';
59
60 --Outputs
61 signal Sand : std_logic;
62 signal Sor : std_logic;
63 signal Sxor : std_logic;
64 signal Sxnor : std_logic;
65 signal SnotA : std_logic;
66 signal SnotB : std_logic;
67 -- No clocks detected in port list. Replace <clock> below with
68 -- appropriate port name
69
70
71
72 BEGIN
73
74     -- Instantiate the Unit Under Test (UUT)

```

```

71
72 BEGIN
73
74     -- Instantiate the Unit Under Test (UUT)
75     uut: Questaol PORT MAP (
76         A => A,
77         B => B,
78         Sand => Sand,
79         Sor => Sor,
80         Sxor => Sxor,
81         Sxnor => Sxnor,
82         SnotA => SnotA,
83         SnotB => SnotB
84     );
85
86
87
88     -- Stimulus process
89     stim_proc: process
90     begin
91         -- hold reset state for 100 ns.
92         wait for 100 ns;
93         A <= '0';
94         B <= '0';
95         wait for 100 ns;
96         A <= '0';
97         B <= '1';
98         wait for 100 ns;
99         A <= '1';
100        B <= '0';
101        wait for 100 ns;
102        A <= '1';
103        B <= '1';

```

## Simulação



## Questão 2.

### Circuito 1

## Módulo

```
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 |
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity Circuit01 is
33     Port ( A : in  STD_LOGIC;
34           B : in  STD_LOGIC;
35           S : out STD_LOGIC);
36 end Circuit01;
37
38 architecture Behavioral of Circuit01 is
39
40 begin
41
42     S <= not(A and B);
43 end Behavioral;
44
```

## Teste

```

35 ENTITY circuitoltest IS
36 END circuitoltest;
37
38 ARCHITECTURE behavior OF circuitoltest IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT Circuitol
43     PORT(
44         A : IN  std_logic;
45         B : IN  std_logic;
46         S : OUT std_logic
47     );
48     END COMPONENT;
49
50
51     --Inputs
52     signal A : std_logic := '0';
53     signal B : std_logic := '0';
54
55     --Outputs
56     signal S : std_logic;
57     -- No clocks detected in port list. Replace <clock> below with
58     -- appropriate port name
59
60
61 BEGIN
62
63     -- Instantiate the Unit Under Test (UUT)
64     uut: Circuitol PORT MAP (

```

BEGIN


```
-- Instantiate the Unit Under Test (UUT)
 uut: Circuit01 PORT MAP (
     A => A,
     B => B,
     S => S
 );

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
    A <= '0';
    B <= '0';
    wait for 100 ns;
    A <= '0';
    B <= '1';
    wait for 100 ns;
    A <= '1';
    B <= '0';
    wait for 100 ns;
    A <= '1';
    B <= '1';

    -- insert stimulus here

    wait;
end process;
```

## Simulação

 

## Circuito 2

## Módulo

```
1
2  entity Circuito2 is
3      Port ( A : in  STD_LOGIC;
4             B : in  STD_LOGIC;
5             C : in  STD_LOGIC;
6             D : in  STD_LOGIC;
7             S : out  STD_LOGIC);
8  end Circuito2;
9
0  architecture Behavioral of Circuito2 is
1
2  begin
3  S <= not ((A and B) or ( C and D));|
4
5
6  end Behavioral;
7
8
```

## Teste



```

34
35 ENTITY Circuito2teste IS
36 END Circuito2teste;
37
38 ARCHITECTURE behavior OF Circuito2teste IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT Circuito2
43     PORT(
44         A : IN  std_logic;
45         B : IN  std_logic;
46         C : IN  std_logic;
47         D : IN  std_logic;
48         S : OUT std_logic
49     );
50     END COMPONENT;
51
52
53     --Inputs
54     signal A : std_logic := '0';
55     signal B : std_logic := '0';
56     signal C : std_logic := '0';
57     signal D : std_logic := '0';
58
59     --Outputs
60     signal S : std_logic;
61     -- No clocks detected in port list. Replace <clock> below with
62     -- appropriate port name
63
64
65 BEGIN
66
67     -- Instantiate the Unit Under Test (UUT)

```

```

65 BEGIN
66
67     -- Instantiate the Unit Under Test (UUT)
68     uut: Circuito2 PORT MAP (
69         A => A,
70         B => B,
71         C => C,
72         D => D,
73         S => S
74     );
75
76
77     -- Stimulus process
78     stim_proc: process
79     begin
80         -- hold reset state for 100 ns.
81         wait for 100 ns;
82         A <= '0';
83         B <= '0';
84         C <= '0';
85         D <= '0';
86         wait for 100 ns;
87         A <= '0';
88         B <= '0';
89         C <= '0';
90         D <= '1';
91         wait for 100 ns;
92         A <= '0';
93         B <= '0';
94         C <= '1';
95         D <= '0';
96         wait for 100 ns;
97         A <= '0';

```

---

```
wait for 100 ns;
A <= '0';
B <= '0';
C <= '1';
D <= '1';
wait for 100 ns;
A <= '0';
B <= '1';
C <= '0';
D <= '0';
wait for 100 ns;
A <= '0';
B <= '1';
C <= '0';
D <= '1';
wait for 100 ns;
A <= '0';
B <= '1';
C <= '1';
D <= '0';
wait for 100 ns;
A <= '0';
B <= '1';
C <= '1';
D <= '1';
wait for 100 ns;
A <= '1';
B <= '0';
C <= '0';
D <= '0';
wait for 100 ns;
A <= '1';
B <= '0';
C <= '0';
```


---

```

131     wait for 100 ns;
132     A <= '1';
133     B <= '0';
134     C <= '1';
135     D <= '0';
136     wait for 100 ns;
137     A <= '1';
138     B <= '0';
139     C <= '1';
140     D <= '1';
141     wait for 100 ns;
142     A <= '1';
143     B <= '1';
144     C <= '0';
145     D <= '0';
146     wait for 100 ns;
147     A <= '1';
148     B <= '1';
149     C <= '0';
150     D <= '1';
151     wait for 100 ns;
152     A <= '1';
153     B <= '1';
154     C <= '1';
155     D <= '0';
156     wait for 100 ns;
157     A <= '1';
158     B <= '1';
159     C <= '1';
160     D <= '1';
161     wait for 100 ns;
162
163

```

## Simulação

 

Questão 3:

Tabela da verdade

A	B	S
0	0	1
0	1	1
1	0	0
1	1	0

Tirando a expressão

$$S = A'B' + A'B$$

Simplificando

$$S = A'(B' + B)$$

$$S = A'$$

Circuito:

