

RELATÓRIO 1 RESOLUÇÃO

QUESTÃO 1

A)

$$S = \overline{\overline{A}B} + [\overline{A}C \oplus (B + C)]$$

B)

Módulo

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Questaol is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          S : out STD_LOGIC);
end Questaol;

architecture Behavioral of Questaol is
    Signal S1,S2,S3,S4: STD_LOGIC;

begin
    S1 <= not(not(A and B));
    S2 <= not(A and C);
    S3 <= C or B;
    S4 <= S2 xor S3;
    S <= S1 or S4;

end Behavioral;
```

Teste


```

41
42     COMPONENT Questaol
43     PORT(
44         A : IN  std_logic;
45         B : IN  std_logic;
46         C : IN  std_logic;
47         S : OUT std_logic
48     );
49     END COMPONENT;
50
51
52     --Inputs
53     signal A : std_logic := '0';
54     signal B : std_logic := '0';
55     signal C : std_logic := '0';
56
57     --Outputs
58     signal S : std_logic;
59     -- No clocks detected in port list. Replace <clock> below with
60     -- appropriate port name
61
62
63
64 BEGIN
65
66     -- Instantiate the Unit Under Test (UUT)
67     uut: Questaol PORT MAP (
68         A => A,
69         B => B,
70         C => C,
71         S => S
72     );

```

```
-- hold reset state for 100 ns.  
wait for 100 ns;  
A <= '0';  
B <= '0';  
C <= '0';  
wait for 100 ns;  
A <= '0';  
B <= '0';  
C <= '1';  
wait for 100 ns;  
A <= '0';  
B <= '1';  
C <= '0';  
wait for 100 ns;  
A <= '0';  
B <= '1';  
C <= '1';  
wait for 100 ns;  
A <= '1';  
B <= '0';  
C <= '0';  
wait for 100 ns;  
A <= '1';  
B <= '0';  
C <= '1';  
wait for 100 ns;  
A <= '1';  
B <= '1';  
C <= '0';  
wait for 100 ns;  
A <= '1';  
B <= '1';  
C <= '1';  
wait for 100 ns;
```

Simulação

 

c)

A	B	C	S
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

D)

$\begin{array}{c c} A & BC \end{array}$	00	01	11	10
0	1	0	0	0
1	1	1	1	1

$$S = A + \overline{B}\overline{C}$$

E)

$$S = \overline{\overline{A}}\overline{\overline{B}} + [\overline{\overline{A}}\overline{\overline{C}} \oplus (B + C)]$$

$$S = AB + [\overline{\overline{A}}\overline{\overline{C}} * (B + C) + \overline{\overline{A}}\overline{\overline{C}} * \overline{(B + C)}]$$

$$S = AB + [ACB + AC + \overline{\overline{A}}\overline{\overline{C}} * (\overline{B}\overline{C})]$$


$$S = AB + [ACB + AC + (\overline{A} + \overline{C})(\overline{B}\overline{C})]$$

$$S = AB + AC + \overline{A}\overline{B}\overline{C} + \overline{B}\overline{C}$$


$$S = AB + AC + \overline{B}\overline{C}$$

$$S = A(B + C) + \overline{B}\overline{C} \xrightarrow{\text{Morgan}} S = A + \overline{B}\overline{C}$$

F) Karnaugh

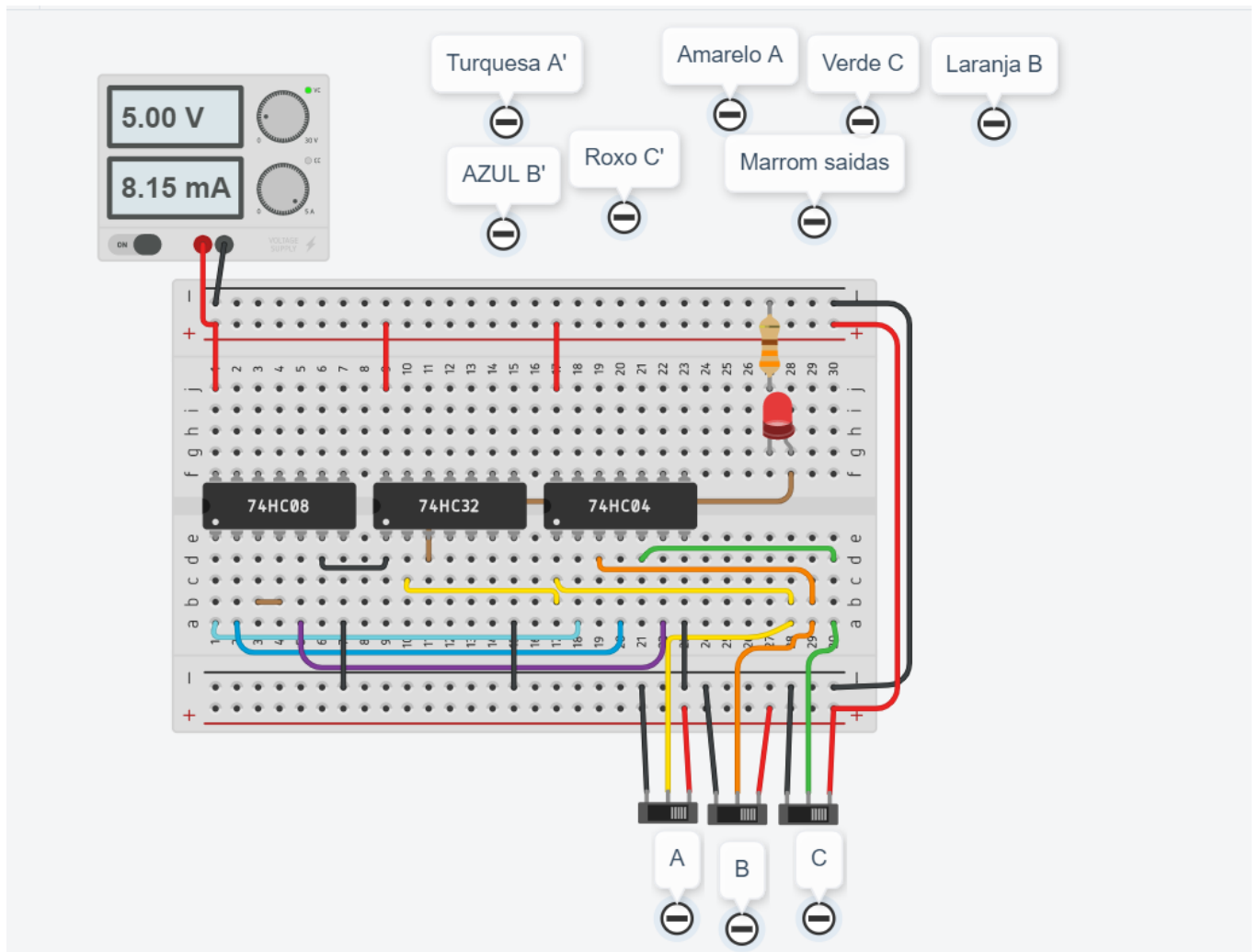

Boole

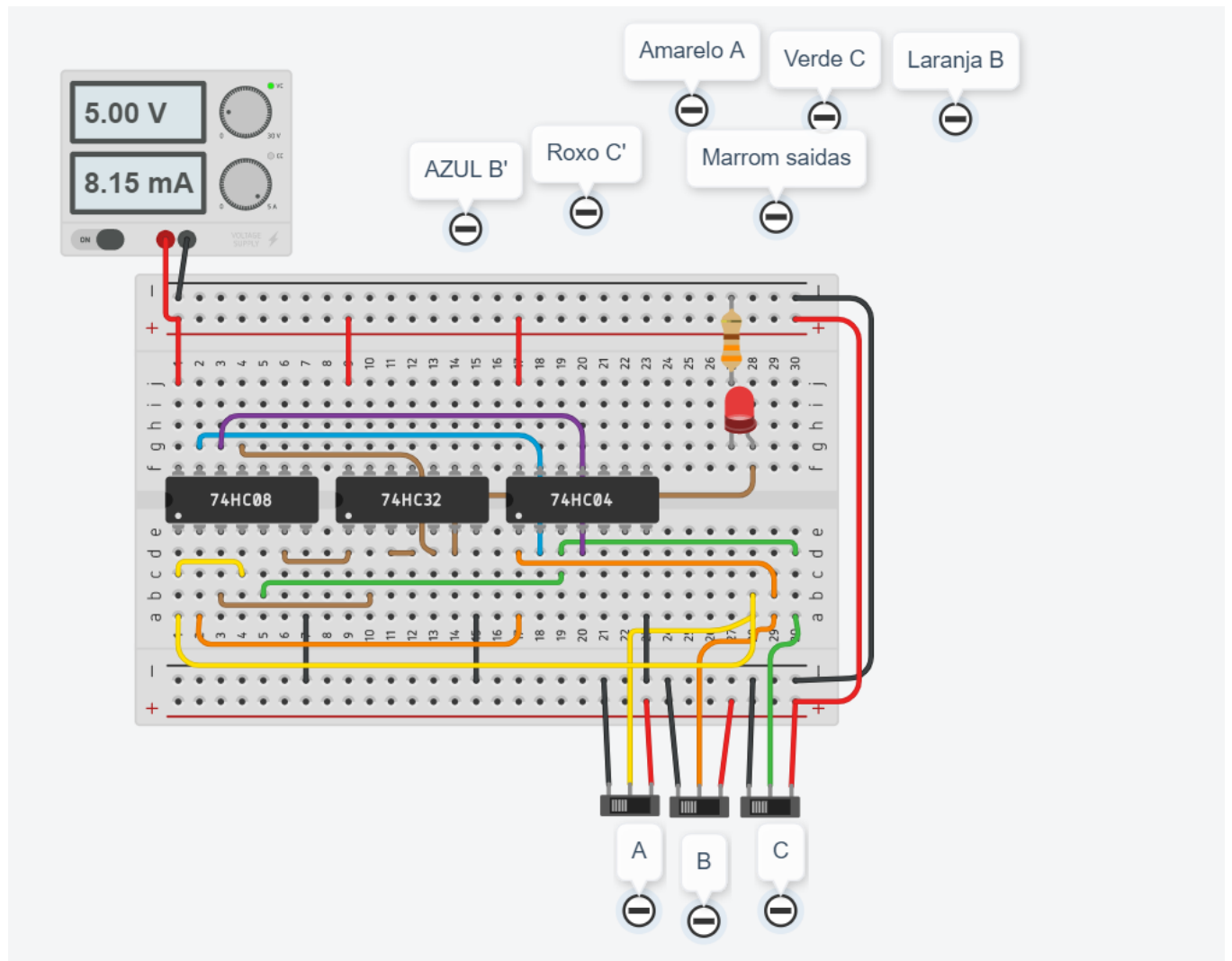

2)

A)

Mux 4:1 com Enable

E	A	B	S
0	0	0	X0
0	0	1	X1
0	1	0	X2
0	1	1	X3
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

B)

Modulo


```

30  --use UNISIM.VComponents.all;
31
32  entity Questo2B is
33      Port ( E : in  STD_LOGIC;
34            A : in  STD_LOGIC;
35            X0 : in  STD_LOGIC;
36            X1 : in  STD_LOGIC;
37            S : out  STD_LOGIC);
38  end Questo2B;
39
40  architecture Behavioral of Questo2B is
41      Signal SX0, SX1: STD_Logic;
42
43  begin
44      SX0 <= not (A) and E and X0;
45      SX1 <= A and E and X1;
46      S <= SX0 or SX1;
47
48
49  end Behavioral;
50

```

Teste

```

34
35 ENTITY Questao2bteste IS
36 END Questao2bteste;
37
38 ARCHITECTURE behavior OF Questao2bteste IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT Questao2B
43     PORT(
44         E : IN  std_logic;
45         A : IN  std_logic;
46         X0 : IN  std_logic;
47         X1 : IN  std_logic;
48         S : OUT std_logic
49     );
50     END COMPONENT;
51
52
53     --Inputs
54     signal E : std_logic := '0';
55     signal A : std_logic := '0';
56     signal X0 : std_logic := '0';
57     signal X1 : std_logic := '0';
58
59     --Outputs
60     signal S : std_logic;
61     -- No clocks detected in port list. Replace <clock> below with
62     -- appropriate port name
63
64
65 BEGIN
66

```

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: Questo2B PORT MAP (

 E => E,

 A => A,

 X0 => X0,

 X1 => X1,

 S => S

);

-- Stimulus process

stim_proc: process

begin

 -- hold reset state for 100 ns.

 wait for 100 ns;

 E <= '0';

 A <= '0';

 X0 <= '0';

 X1 <= '0';

 wait for 100 ns;

 E <= '0';

 A <= '0';

 X0 <= '1';

 X1 <= '0';

 wait for 100 ns;

 E <= '0';

 A <= '1';

 X0 <= '0';

 X1 <= '1';


 wait for 100 ns;

```

93     wait for 100 ns;
94     E <= '0';
95     A <= '1';
96     X0 <= '0';
97     X1 <= '1';
98     wait for 100 ns;
99     E <= '1';
100    A <= '0';
101    X0 <= '0';
102    X1 <= '0';
103    wait for 100 ns;
104    E <= '1';
105    A <= '0';
106    X0 <= '1';
107    X1 <= '0';
108    wait for 100 ns;
109    E <= '1';
110    A <= '1';
111    X0 <= '0';
112    X1 <= '0';
113    wait for 100 ns;
114    E <= '1';
115    A <= '1';
116    X0 <= '0';
117    X1 <= '1';|
118
119
120
121    -- insert stimulus here
122
123    wait;
124 end process;
125
126 END;

```

Simulação

 

C)

Modulo

```
31
32 entity Questao2C is
33     Port ( E : in  STD_LOGIC;
34           A : in  STD_LOGIC;
35           X0 : in  STD_LOGIC;
36           X1 : in  STD_LOGIC;
37           S : out  STD_LOGIC);
38 end Questao2C;
39
40 architecture Behavioral of Questao2C is
41
42
43 begin
44     process(E,A,X0,X1)
45     begin
46         if(E = '0') THEN
47             S <= '0';
48         else
49             if(A = '0') THEN
50                 S <= X0;
51             else
52                 S <= X1;
53             end if;
54
55         end if;
56     end process;
57
58
```


Teste

```

-- hold reset state for 100 ns.
wait for 100 ns;
E <= '0';
A <= '0';
X0 <= '0';
X1 <= '0';
wait for 100 ns;
E <= '0';
A <= '0';
X0 <= '1';
X1 <= '0';
wait for 100 ns;
E <= '0';
A <= '1';
X0 <= '0';
X1 <= '1';
wait for 100 ns;
E <= '1';
A <= '0';
X0 <= '0';
X1 <= '0';
wait for 100 ns;
E <= '1';
A <= '0';
X0 <= '1';
X1 <= '0';
wait for 100 ns;
E <= '1';
A <= '1';
X0 <= '0';
X1 <= '0';
wait for 100 ns;
E <= '1';
A <= '1';
X0 <= '0';
X1 <= '0';
wait for 100 ns;
E <= '1';
A <= '1';
X0 <= '0';
X1 <= '1';

```

Simulação

 

D)

